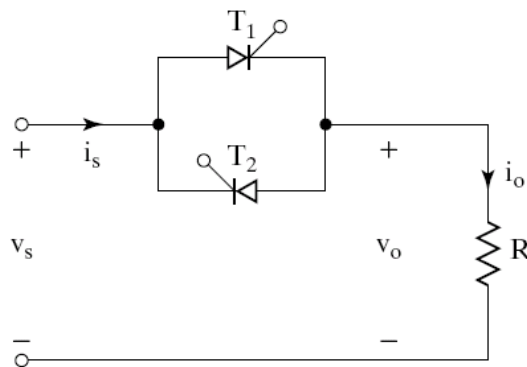


## SINGLE PHASE FULL WAVE AC VOLTAGE CONTROLLER (AC REGULATOR)

Single phase full wave ac voltage controller circuit using two SCRs or a single triac is generally used in most of the ac control applications. The ac power flow to the load can be controlled in both the half cycles by varying the trigger angle ' $\alpha$ '.

The RMS value of load voltage can be varied by varying the trigger angle ' $\alpha$ '. The input supply current is alternating in the case of a full wave ac voltage controller and due to the symmetrical nature of the input supply current waveform there is no dc component of input supply current i.e., the average value of the input supply current is zero.

A single phase full wave ac voltage controller with a resistive load is shown in the figure below. It is possible to control the ac power flow to the load in both the half cycles by adjusting the trigger angle ' $\alpha$ '. Hence the full wave ac voltage controller is also referred to as to a bi-directional controller.




**Fig.:** Single phase full wave ac voltage controller (Bi-directional Controller) using SCRs

The thyristor  $T_1$  is forward biased during the positive half cycle of the input supply voltage. The thyristor  $T_1$  is triggered at a delay angle of ' $\alpha$ ' ( $0 \leq \alpha \leq \pi$  radians). Considering the ON thyristor  $T_1$  as an ideal closed switch the input supply voltage appears across the load resistor  $R_L$  and the output voltage  $v_o = v_s$  during  $\omega t = \alpha$  to  $\pi$  radians. The load current flows through the ON thyristor  $T_1$  and through the load resistor  $R_L$  in the downward direction during the conduction time of  $T_1$  from  $\omega t = \alpha$  to  $\pi$  radians.


At  $\omega t = \pi$ , when the input voltage falls to zero the thyristor current (which is flowing through the load resistor  $R_L$ ) falls to zero and hence  $T_1$  naturally turns off. No current flows in the circuit during  $\omega t = \pi$  to  $(\pi + \alpha)$ .

The thyristor  $T_2$  is forward biased during the negative cycle of input supply and when thyristor  $T_2$  is triggered at a delay angle  $(\pi + \alpha)$ , the output voltage follows the negative halfcycle of input from  $\omega t = (\pi + \alpha)$  to  $2\pi$ . When  $T_2$  is ON, the load current flows in the reverse direction (upward direction) through  $T_2$  during  $\omega t = (\pi + \alpha)$  to  $2\pi$  radians. The time interval (spacing) between the gate trigger pulses of  $T_1$  and  $T_2$  is kept at  $\pi$  radians or  $180^\circ$ . At  $\omega t = 2\pi$  the input supply voltage falls to zero and hence the load current also falls to zero and thyristor  $T_2$  turn off naturally.

*Instead of using two SCR's in parallel, a Triac can be used for full wave ac voltage control.*

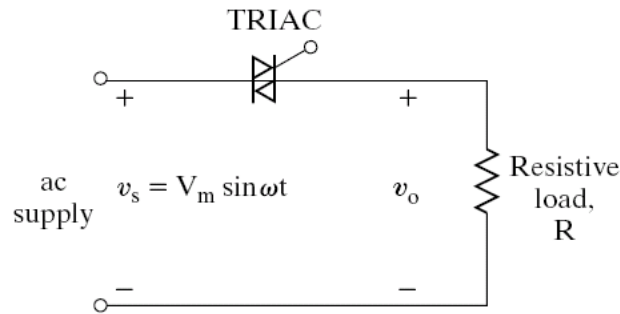

**Fig.: Single phase full wave ac voltage controller (Bi-directional Controller) using TRIAC**

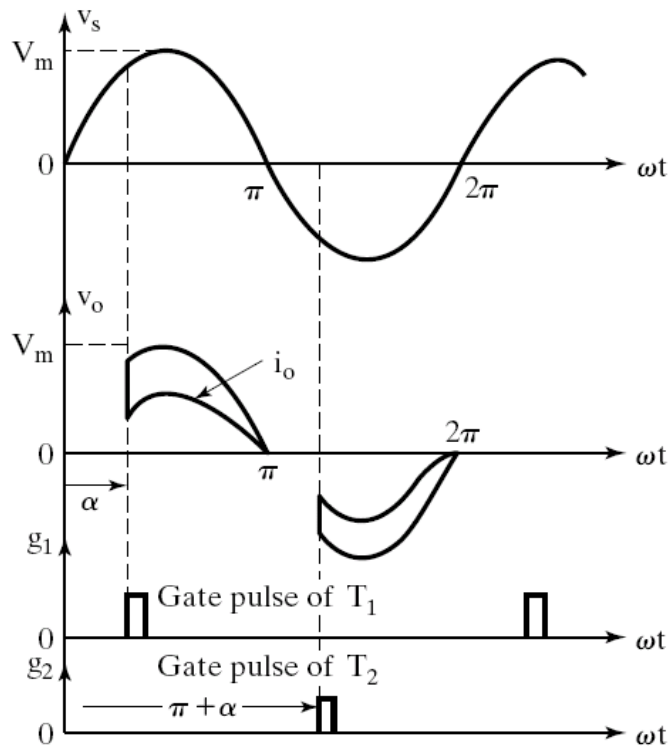

**Fig: Waveforms of single phase full wave ac voltage controller**

**EQUATIONS****Input supply voltage**

$$v_s = V_m \sin \omega t = \sqrt{2}V_s \sin \omega t ;$$

**Output voltage across the load resistor  $R_L$  ;**

$$v_o = v_L = V_m \sin \omega t ;$$

for  $\omega t = \alpha$  to  $\pi$  and  $\omega t = (\pi + \alpha)$  to  $2\pi$

**Output load current**

$$i_o = \frac{v_o}{R_L} = \frac{V_m \sin \omega t}{R_L} = I_m \sin \omega t ;$$

for  $\omega t = \alpha$  to  $\pi$  and  $\omega t = (\pi + \alpha)$  to  $2\pi$

**TO DERIVE AN EXPRESSION FOR THE RMS VALUE OF OUTPUT (LOAD) VOLTAGE**

The RMS value of output voltage (load voltage) can be found using the expression

$$V_{O(RMS)}^2 = V_{L(RMS)}^2 = \frac{1}{2\pi} \int_0^{2\pi} v_L^2 d(\omega t) ;$$

For a full wave ac voltage controller, we can see that the two half cycles of output voltage waveforms are symmetrical and the output pulse time period (or output pulse repetition time) is  $\pi$  radians. Hence we can also calculate the RMS output voltage by using the expression given below.

$$V_{L(RMS)}^2 = \frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t d\omega t$$

$$V_{L(RMS)}^2 = \frac{1}{2\pi} \int_0^{2\pi} v_L^2 d(\omega t) ;$$

$v_L = v_o = V_m \sin \omega t$  ; For  $\omega t = \alpha$  to  $\pi$  and  $\omega t = (\pi + \alpha)$  to  $2\pi$

Hence,

$$\begin{aligned} V_{L(RMS)}^2 &= \frac{1}{2\pi} \left[ \int_{\alpha}^{\pi} (V_m \sin \omega t)^2 d(\omega t) + \int_{\pi+\alpha}^{2\pi} (V_m \sin \omega t)^2 d(\omega t) \right] \\ &= \frac{1}{2\pi} \left[ V_m^2 \int_{\alpha}^{\pi} \sin^2 \omega t d(\omega t) + V_m^2 \int_{\pi+\alpha}^{2\pi} \sin^2 \omega t d(\omega t) \right] \\ &= \frac{V_m^2}{2\pi} \left[ \int_{\alpha}^{\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t) + \int_{\pi+\alpha}^{2\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t) \right] \end{aligned}$$

$$\begin{aligned}
&= \frac{V_m^2}{2\pi \times 2} \left[ \int_{\alpha}^{\pi} d(\omega t) - \int_{\alpha}^{\pi} \cos 2\omega t \cdot d(\omega t) + \int_{\pi+\alpha}^{2\pi} d(\omega t) - \int_{\pi+\alpha}^{2\pi} \cos 2\omega t \cdot d(\omega t) \right] \\
&= \frac{V_m^2}{4\pi} \left[ (\omega t) \Big|_{\alpha}^{\pi} + (\omega t) \Big|_{\pi+\alpha}^{2\pi} - \left[ \frac{\sin 2\omega t}{2} \right]_{\alpha}^{\pi} - \left[ \frac{\sin 2\omega t}{2} \right]_{\pi+\alpha}^{2\pi} \right] \\
&= \frac{V_m^2}{4\pi} \left[ (\pi - \alpha) + (\pi - \alpha) - \frac{1}{2}(\sin 2\pi - \sin 2\alpha) - \frac{1}{2}(\sin 4\pi - \sin 2(\pi + \alpha)) \right] \\
&= \frac{V_m^2}{4\pi} \left[ 2(\pi - \alpha) - \frac{1}{2}(0 - \sin 2\alpha) - \frac{1}{2}(0 - \sin 2(\pi + \alpha)) \right] \\
&= \frac{V_m^2}{4\pi} \left[ 2(\pi - \alpha) + \frac{\sin 2\alpha}{2} + \frac{\sin 2(\pi + \alpha)}{2} \right] \\
&= \frac{V_m^2}{4\pi} \left[ 2(\pi - \alpha) + \frac{\sin 2\alpha}{2} + \frac{\sin(2\pi + 2\alpha)}{2} \right] \\
&= \frac{V_m^2}{4\pi} \left[ 2(\pi - \alpha) + \frac{\sin 2\alpha}{2} + \frac{1}{2}(\sin 2\pi \cdot \cos 2\alpha + \cos 2\pi \cdot \sin 2\alpha) \right] \\
&\sin 2\pi = 0 \quad \& \quad \cos 2\pi = 1
\end{aligned}$$

Therefore,

$$\begin{aligned}
V_{L(RMS)}^2 &= \frac{V_m^2}{4\pi} \left[ 2(\pi - \alpha) + \frac{\sin 2\alpha}{2} + \frac{\sin 2\alpha}{2} \right] \\
&= \frac{V_m^2}{4\pi} [2(\pi - \alpha) + \sin 2\alpha] \\
V_{L(RMS)}^2 &= \frac{V_m^2}{4\pi} [(2\pi - 2\alpha) + \sin 2\alpha]
\end{aligned}$$

Taking the square root, we get

$$\begin{aligned}
V_{L(RMS)} &= \frac{V_m}{2\sqrt{\pi}} \sqrt{[(2\pi - 2\alpha) + \sin 2\alpha]} \\
V_{L(RMS)} &= \frac{V_m}{\sqrt{2}\sqrt{2\pi}} \sqrt{[(2\pi - 2\alpha) + \sin 2\alpha]}
\end{aligned}$$

$$V_{L(RMS)} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{2\pi} [(2\pi - 2\alpha) + \sin 2\alpha]}$$

$$V_{L(RMS)} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{2\pi} \left[ 2 \left\{ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right\} \right]}$$

$$V_{L(RMS)} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}$$

$$V_{L(RMS)} = V_{i(RMS)} \sqrt{\frac{1}{\pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}$$

$$V_{L(RMS)} = V_s \sqrt{\frac{1}{\pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}$$

Maximum RMS voltage will be applied to the load when  $\alpha = 0$ , in that case the full sine wave appears across the load. RMS load voltage will be the same as the RMS supply voltage  $= \frac{V_m}{\sqrt{2}}$ . When  $\alpha$  is increased the RMS load voltage decreases.

$$V_{L(RMS)} \Big|_{\alpha=0} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} \left[ (\pi - 0) + \frac{\sin 2 \times 0}{2} \right]}$$

$$V_{L(RMS)} \Big|_{\alpha=0} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} \left[ (\pi) + \frac{0}{2} \right]}$$

$$V_{L(RMS)} \Big|_{\alpha=0} = \frac{V_m}{\sqrt{2}} = V_{i(RMS)} = V_s$$

The output control characteristic for a single phase full wave ac voltage controller with resistive load can be obtained by plotting the equation for  $V_{O(RMS)}$


### **CONTROL CHARACTERISTIC OF SINGLE PHASE FULL-WAVE AC VOLTAGE CONTROLLER WITH RESISTIVE LOAD**

The control characteristic is the plot of RMS output voltage  $V_{O(RMS)}$  versus the trigger angle  $\alpha$ ; which can be obtained by using the expression for the RMS output voltage of a full-wave ac controller with resistive load.

$$V_{O(RMS)} = V_s \sqrt{\frac{1}{\pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]} \quad ;$$

Where  $V_s = \frac{V_m}{\sqrt{2}}$  = RMS value of input supply voltage


Trigger angle $\alpha$ in degrees	Trigger angle $\alpha$ in radians	$V_{O(RMS)}$	%
0	0	$V_s$	100% $V_s$
30°	$\frac{\pi}{6}$ ; ( $\frac{1\pi}{6}$ )	0.985477 $V_s$	98.54% $V_s$
60°	$\frac{\pi}{3}$ ; ( $\frac{2\pi}{6}$ )	0.896938 $V_s$	89.69% $V_s$
90°	$\frac{\pi}{2}$ ; ( $\frac{3\pi}{6}$ )	0.7071 $V_s$	70.7% $V_s$
120°	$\frac{2\pi}{3}$ ; ( $\frac{4\pi}{6}$ )	0.44215 $V_s$	44.21% $V_s$
150°	$\frac{5\pi}{6}$ ; ( $\frac{5\pi}{6}$ )	0.1698 $V_s$	16.98% $V_s$
180°	$\pi$ ; ( $\frac{6\pi}{6}$ )	0 $V_s$	0 $V_s$

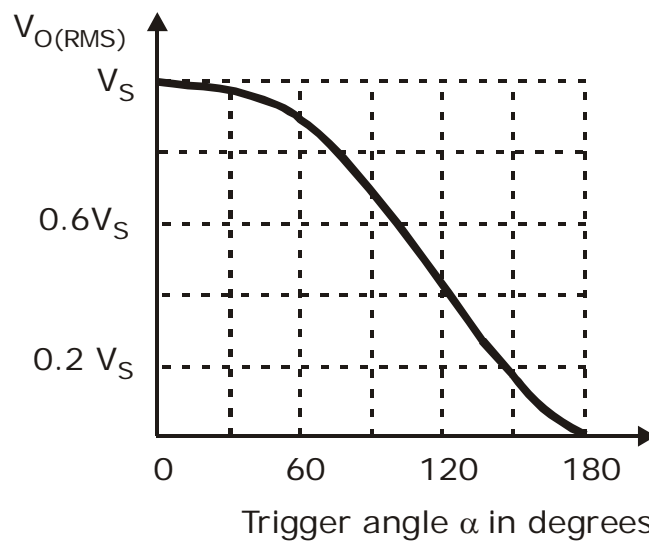

We can notice from the figure, that we obtain a much better output control characteristic by using a single phase full wave ac voltage controller. The RMS output voltage can be varied from a maximum of 100%  $V_s$  at  $\alpha = 0$  to a minimum of '0' at  $\alpha = 180^\circ$ . Thus we get a full range output voltage control by using a single phase full wave ac voltage controller.

### Need For Isolation


In the single phase full wave ac voltage controller circuit using two SCRs or Thyristors  $T_1$  and  $T_2$  in parallel, the gating circuits (gate trigger pulse generating circuits) of Thyristors  $T_1$  and  $T_2$  must be isolated. Figure shows a pulse transformer with two separate windings to provide isolation between the gating signals of  $T_1$  and  $T_2$ .

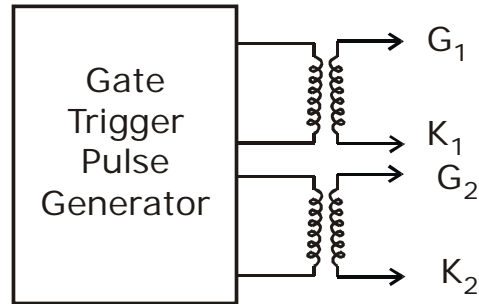

**Fig.: Pulse Transformer**

### SINGLE PHASE FULL-WAVE AC VOLTAGE CONTROLLER WITH COMMON CATHODE

It is possible to design a single phase full wave ac controller with a common cathode configuration by having a common cathode point for  $T_1$  and  $T_2$  & by adding two diodes in a full wave ac controller circuit as shown in the figure below

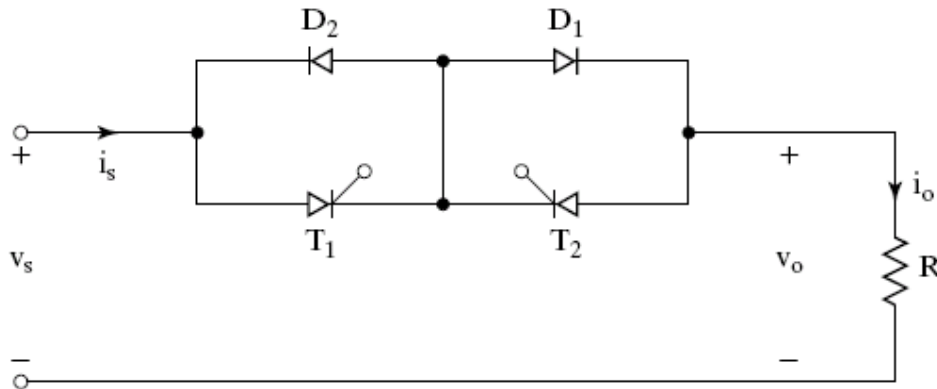

**Fig.: Single phase full wave ac controller with common cathode  
(Bidirectional controller in common cathode configuration)**


Thyristor  $T_1$  and diode  $D_1$  are forward biased during the positive half cycle of input supply. When thyristor  $T_1$  is triggered at a delay angle  $\alpha$ , Thyristor  $T_1$  and diode  $D_1$  conduct together from  $\omega t = \alpha$  to  $\pi$  during the positive half cycle.

The thyristor  $T_2$  and diode  $D_2$  are forward biased during the negative half cycle of input supply, when triggered at a delay angle  $\alpha$ , thyristor  $T_2$  and diode  $D_2$  conduct together during the negative half cycle from  $\omega t = (\pi + \alpha)$  to  $2\pi$ .

In this circuit as there is one single common cathode point, routing of the gate trigger pulses to the thyristor gates of  $T_1$  and  $T_2$  is simpler and only one isolation circuit is required.

But due to the need of two power diodes the costs of the devices increase. As there are two power devices conducting at the same time the voltage drop across the ON devices increases and the ON state conducting losses of devices increase and hence the efficiency decreases.
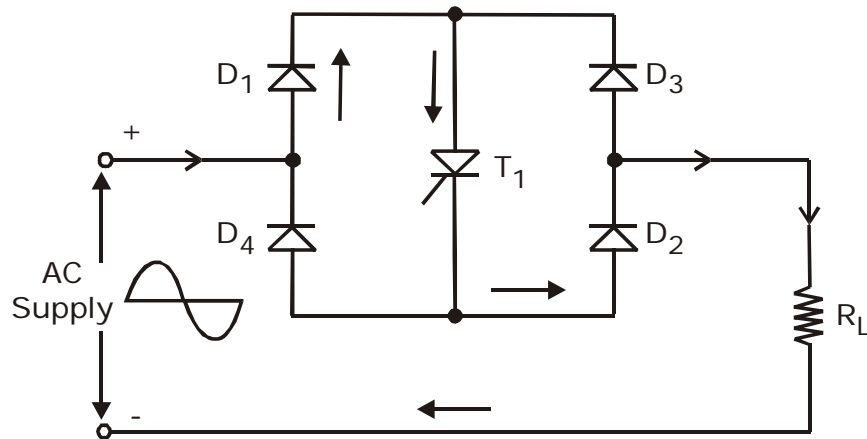
## SINGLE PHASE FULL WAVE AC VOLTAGE CONTROLLER USING A SINGLE THYRISTOR



A single phase full wave ac controller can also be implemented with one thyristor and four diodes connected in a full wave bridge configuration as shown in the above figure. The four diodes act as a bridge full wave rectifier. The voltage across the thyristor  $T_1$  and current through thyristor  $T_1$  are always unidirectional. When  $T_1$  is triggered at  $\omega t = \alpha$ , during the positive half cycle ( $0 \leq \alpha \leq \pi$ ), the load current flows through  $D_1$ ,  $T_1$ , diode  $D_2$  and through the load. With a resistive load, the thyristor current (flowing through the ON thyristor  $T_1$ ), the load current falls to zero at  $\omega t = \pi$ , when the input supply voltage decreases to zero at  $\omega t = \pi$ , the thyristor naturally turns OFF.

In the negative half cycle, diodes  $D_3$  &  $D_4$  are forward biased during  $\omega t = \pi$  to  $2\pi$  radians. When  $T_1$  is triggered at  $\omega t = (\pi + \alpha)$ , the load current flows in the opposite direction (upward direction) through the load, through  $D_3$ ,  $T_1$  and  $D_4$ . Thus  $D_3$ ,  $D_4$  and  $T_1$  conduct together during the negative half cycle to supply the load power. When the input supply voltage becomes zero at  $\omega t = 2\pi$ , the thyristor current (load current) falls to zero at  $\omega t = 2\pi$  and the thyristor  $T_1$  naturally turns OFF. The waveforms and the expression for the RMS output voltage are the same as discussed earlier for the single phase full wave ac controller.

But however if there is a large inductance in the load circuit, thyristor  $T_1$  may not be turned OFF at the zero crossing points, in every half cycle of input voltage and this may result in a loss of output control. This would require detection of the zero crossing of the load current waveform in order to ensure guaranteed turn off of the conducting thyristor before triggering the thyristor in the next half cycle, so that we gain control on the output voltage.

In this full wave ac controller circuit using a single thyristor, as there are three power devices conducting together at the same time there is more conduction voltage drop and an increase in the ON state conduction losses and hence efficiency is also reduced.

The diode bridge rectifier and thyristor (or a power transistor) act together as a bidirectional switch which is commercially available as a single device module and it has




relatively low ON state conduction loss. It can be used for bidirectional load current control and for controlling the RMS output voltage.

### **SINGLE PHASE FULL WAVE AC VOLTAGE CONTROLLER (BIDIRECTIONAL CONTROLLER) WITH RL LOAD**

In this section we will discuss the operation and performance of a single phase full wave ac voltage controller with RL load. In practice most of the loads are of RL type. For example if we consider a single phase full wave ac voltage controller controlling the speed of a single phase ac induction motor, the load which is the induction motor winding is an RL type of load, where R represents the motor winding resistance and L represents the motor winding inductance.

A single phase full wave ac voltage controller circuit (bidirectional controller) with an RL load using two thyristors  $T_1$  and  $T_2$  ( $T_1$  and  $T_2$  are two SCRs) connected in parallel is shown in the figure below. In place of two thyristors a single Triac can be used to implement a full wave ac controller, if a suitable Triac is available for the desired RMS load current and the RMS output voltage ratings.

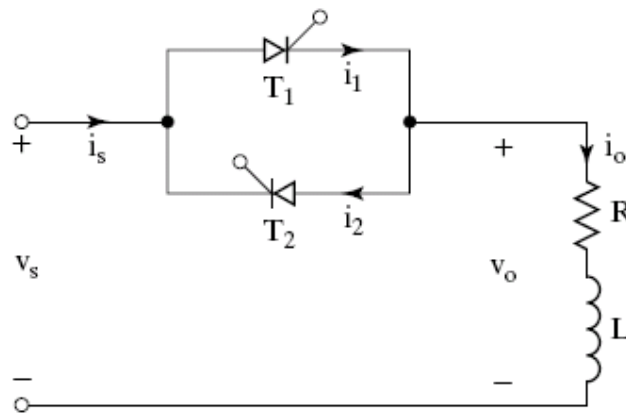


**Fig: Single phase full wave ac voltage controller with RL load**

The thyristor  $T_1$  is forward biased during the positive half cycle of input supply. Let us assume that  $T_1$  is triggered at  $\omega t = \alpha$ , by applying a suitable gate trigger pulse to  $T_1$  during the positive half cycle of input supply. The output voltage across the load follows the input supply voltage when  $T_1$  is ON. The load current  $i_o$  flows through the thyristor  $T_1$  and through the load in the downward direction. This load current pulse flowing through  $T_1$  can be considered as the positive current pulse. Due to the inductance

in the load, the load current  $i_o$  flowing through  $T_1$  would not fall to zero at  $\omega t = \pi$ , when the input supply voltage starts to become negative.

The thyristor  $T_1$  will continue to conduct the load current until all the inductive energy stored in the load inductor  $L$  is completely utilized and the load current through  $T_1$  falls to zero at  $\omega t = \beta$ , where  $\beta$  is referred to as the Extinction angle, (the value of  $\omega t$ ) at which the load current falls to zero. The extinction angle  $\beta$  is measured from the point of the beginning of the positive half cycle of input supply to the point where the load current falls to zero.

The thyristor  $T_1$  conducts from  $\omega t = \alpha$  to  $\beta$ . The conduction angle of  $T_1$  is  $\delta = (\beta - \alpha)$ , which depends on the delay angle  $\alpha$  and the load impedance angle  $\phi$ . The waveforms of the input supply voltage, the gate trigger pulses of  $T_1$  and  $T_2$ , the thyristor current, the load current and the load voltage waveforms appear as shown in the figure below.

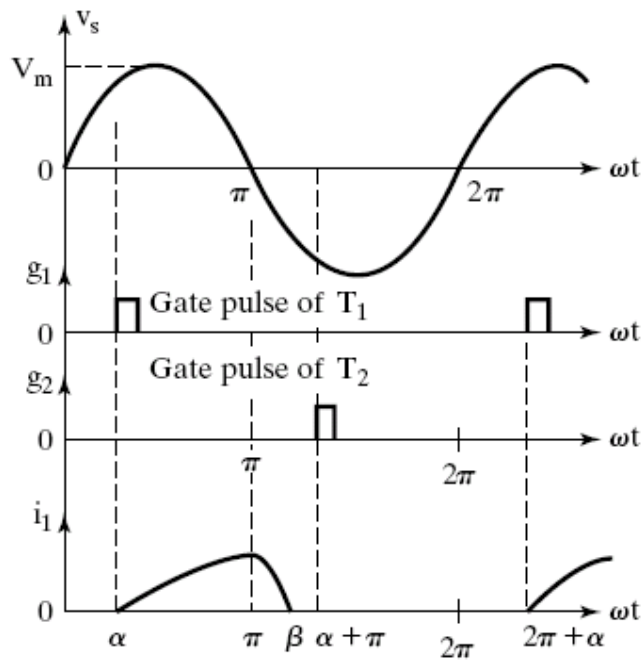

**Fig.: Input supply voltage & Thyristor current waveforms**

$\beta$  is the extinction angle which depends upon the load inductance value.



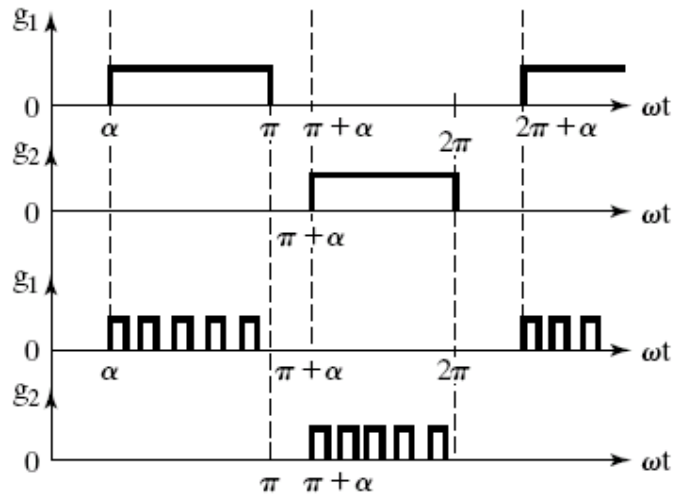


Fig.: Gating Signals

Waveforms of single phase full wave ac voltage controller with RL load for  $\alpha > \phi$ .  
 Discontinuous load current operation occurs for  $\alpha > \phi$  and  $\beta < (\pi + \alpha)$ ;  
 i.e.,  $(\beta - \alpha) < \pi$ , conduction angle  $< \pi$ .

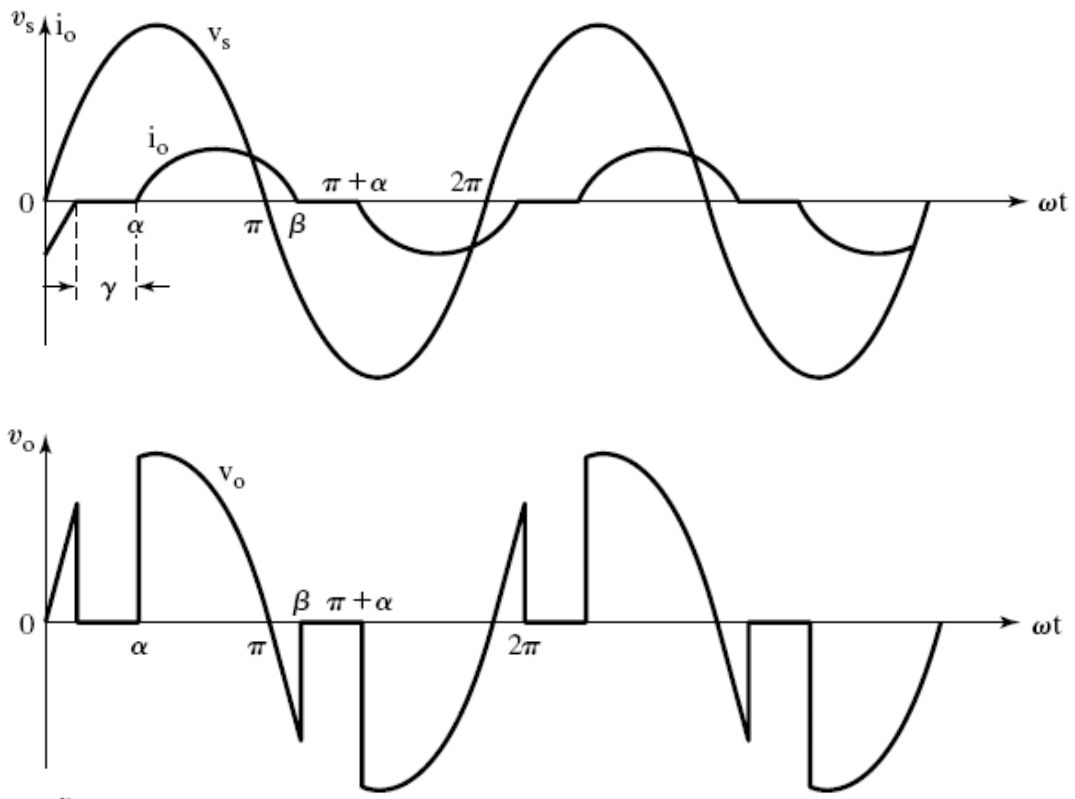

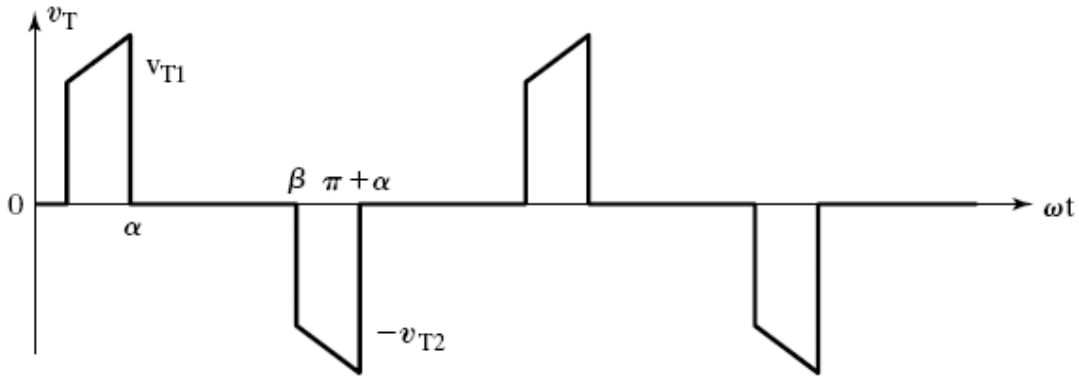

**Fig.: Waveforms of Input supply voltage, Load Current, Load Voltage and Thyristor Voltage across  $T_1$**

**Note**

- The RMS value of the output voltage and the load current may be varied by varying the trigger angle  $\alpha$ .
- This circuit, AC RMS voltage controller can be used to regulate the RMS voltage across the terminals of an ac motor (induction motor). It can be used to control the temperature of a furnace by varying the RMS output voltage.
- For very large load inductance 'L' the SCR may fail to commute, after it is triggered and the load voltage will be a full sine wave (similar to the applied input supply voltage and the output control will be lost) as long as the gating signals are applied to the thyristors  $T_1$  and  $T_2$ . The load current waveform will appear as a full continuous sine wave and the load current waveform lags behind the output sine wave by the load power factor angle  $\phi$ .

**TO DERIVE AN EXPRESSION FOR THE OUTPUT (INDUCTIVE LOAD) CURRENT, DURING  $\omega t = \alpha$  to  $\beta$  WHEN THYRISTOR  $T_1$  CONDUCTS**

Considering sinusoidal input supply voltage we can write the expression for the supply voltage as

$$v_s = V_m \sin \omega t = \text{instantaneous value of the input supply voltage.}$$

Let us assume that the thyristor  $T_1$  is triggered by applying the gating signal to  $T_1$  at  $\omega t = \alpha$ . The load current which flows through the thyristor  $T_1$  during  $\omega t = \alpha$  to  $\beta$  can be found from the equation

$$L \left( \frac{di_o}{dt} \right) + Ri_o = V_m \sin \omega t ;$$

The solution of the above differential equation gives the general expression for the output load current which is of the form

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-t}{\tau}} ;$$

Where  $V_m = \sqrt{2}V_s =$  maximum or peak value of input supply voltage.

$$Z = \sqrt{R^2 + (\omega L)^2} = \text{Load impedance.}$$

$$\phi = \tan^{-1} \left( \frac{\omega L}{R} \right) = \text{Load impedance angle (power factor angle of load).}$$

$$\tau = \frac{L}{R} = \text{Load circuit time constant.}$$

Therefore the general expression for the output load current is given by the equation

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-R}{L} t} ;$$

The value of the constant  $A_1$  can be determined from the initial condition. i.e. initial value of load current  $i_o = 0$ , at  $\omega t = \alpha$ . Hence from the equation for  $i_o$  equating  $i_o$  to zero and substituting  $\omega t = \alpha$ , we get

$$i_o = 0 = \frac{V_m}{Z} \sin(\alpha - \phi) + A_1 e^{\frac{-R}{L} t}$$

Therefore  $A_1 e^{\frac{-R}{L} t} = -\frac{V_m}{Z} \sin(\alpha - \phi)$

$$A_1 = \frac{1}{e^{\frac{-R}{L} t}} \left[ -\frac{V_m}{Z} \sin(\alpha - \phi) \right]$$

$$A_1 = e^{\frac{+R}{L} t} \left[ -\frac{V_m}{Z} \sin(\alpha - \phi) \right]$$

$$A_1 = e^{\frac{R(\omega t)}{\omega L}} \left[ -\frac{V_m}{Z} \sin(\alpha - \phi) \right]$$

By substituting  $\omega t = \alpha$ , we get the value of constant  $A_1$  as

$$A_1 = e^{\frac{R(\alpha)}{\omega L}} \left[ -\frac{V_m}{Z} \sin(\alpha - \phi) \right]$$

Substituting the value of constant  $A_1$  from the above equation into the expression for  $i_o$ , we obtain

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + e^{\frac{-R}{L} t} e^{\frac{R(\alpha)}{\omega L}} \left[ \frac{-V_m}{Z} \sin(\alpha - \phi) \right] ;$$

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + e^{\frac{-R(\omega t)}{\omega L}} e^{\frac{R(\alpha)}{\omega L}} \left[ \frac{-V_m}{Z} \sin(\alpha - \phi) \right]$$

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + e^{\frac{-R(\omega t - \alpha)}{\omega L}} \left[ \frac{-V_m}{Z} \sin(\alpha - \phi) \right]$$

Therefore we obtain the final expression for the inductive load current of a single phase full wave ac voltage controller with RL load as

$$i_o = \frac{V_m}{Z} \left[ \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R(\omega t - \alpha)}{\omega L}} \right] ; \quad \text{Where } \alpha \leq \omega t \leq \beta .$$

The above expression also represents the thyristor current  $i_{T1}$ , during the conduction time interval of thyristor  $T_1$  from  $\omega t = \alpha$  to  $\beta$ .

#### To Calculate Extinction Angle $\beta$

The extinction angle  $\beta$ , which is the value of  $\omega t$  at which the load current  $i_o$  falls to zero and  $T_1$  is turned off can be estimated by using the condition that  $i_o = 0$ , at  $\omega t = \beta$

By using the above expression for the output load current, we can write

$$i_o = 0 = \frac{V_m}{Z} \left[ \sin(\beta - \phi) - \sin(\alpha - \phi) e^{\frac{-R(\beta - \alpha)}{\omega L}} \right]$$

As  $\frac{V_m}{Z} \neq 0$  we can write

$$\left[ \sin(\beta - \phi) - \sin(\alpha - \phi) e^{\frac{-R(\beta - \alpha)}{\omega L}} \right] = 0$$

Therefore we obtain the expression

$$\sin(\beta - \phi) = \sin(\alpha - \phi) e^{\frac{-R(\beta - \alpha)}{\omega L}}$$

The extinction angle  $\beta$  can be determined from this transcendental equation by using the iterative method of solution (trial and error method). After  $\beta$  is calculated, we can determine the thyristor conduction angle  $\delta = (\beta - \alpha)$ .

$\beta$  is the extinction angle which depends upon the load inductance value. Conduction angle  $\delta$  increases as  $\alpha$  is decreased for a known value of  $\beta$ .

For  $\delta < \pi$  radians, i.e., for  $(\beta - \alpha) < \pi$  radians, for  $(\pi + \alpha) > \beta$  the load current waveform appears as a discontinuous current waveform as shown in the figure. The output load current remains at zero during  $\omega t = \beta$  to  $(\pi + \alpha)$ . This is referred to as discontinuous load current operation which occurs for  $\beta < (\pi + \alpha)$ .


When the trigger angle  $\alpha$  is decreased and made equal to the load impedance angle  $\phi$  i.e., when  $\alpha = \phi$  we obtain from the expression for  $\sin(\beta - \phi)$ ,

$$\sin(\beta - \phi) = 0 \quad ; \quad \text{Therefore } (\beta - \phi) = \pi \text{ radians.}$$

**Extinction angle**  $\beta = (\pi + \phi) = (\pi + \alpha)$  ; for the case when  $\alpha = \phi$

**Conduction angle**  $\delta = (\beta - \alpha) = \pi \text{ radians} = 180^\circ$  ; for the case when  $\alpha = \phi$

Each thyristor conducts for  $180^\circ$  ( $\pi$  radians) .  $T_1$  conducts from  $\omega t = \phi$  to  $(\pi + \phi)$  and provides a positive load current.  $T_2$  conducts from  $(\pi + \phi)$  to  $(2\pi + \phi)$  and provides a negative load current. Hence we obtain a continuous load current and the output voltage waveform appears as a continuous sine wave identical to the input supply voltage waveform for trigger angle  $\alpha \leq \phi$  and the control on the output is lost.

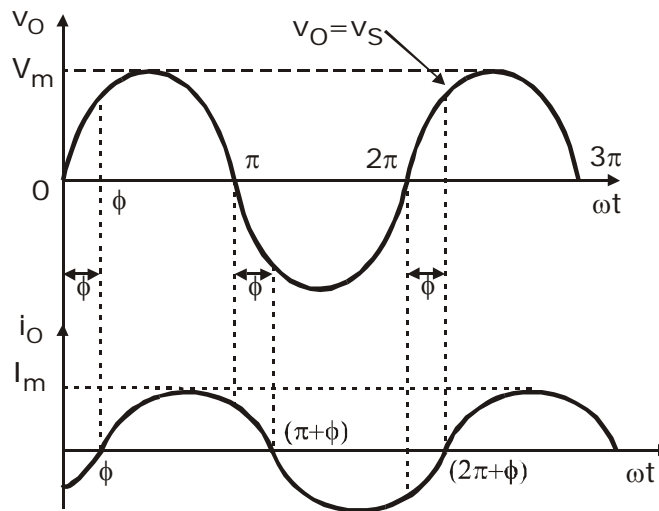

**Fig.: Output voltage and output current waveforms for a single phase full wave ac voltage controller with RL load for  $\alpha \leq \phi$**


Thus we observe that for trigger angle  $\alpha \leq \phi$ , the load current tends to flow continuously and we have continuous load current operation, without any break in the load current waveform and we obtain output voltage waveform which is a continuous sinusoidal waveform identical to the input supply voltage waveform. We lose the control on the output voltage for  $\alpha \leq \phi$  as the output voltage becomes equal to the input supply voltage and thus we obtain

$$V_{O(RMS)} = \frac{V_m}{\sqrt{2}} = V_s \quad ; \text{ for } \alpha \leq \phi$$

Hence,

RMS output voltage = RMS input supply voltage for  $\alpha \leq \phi$

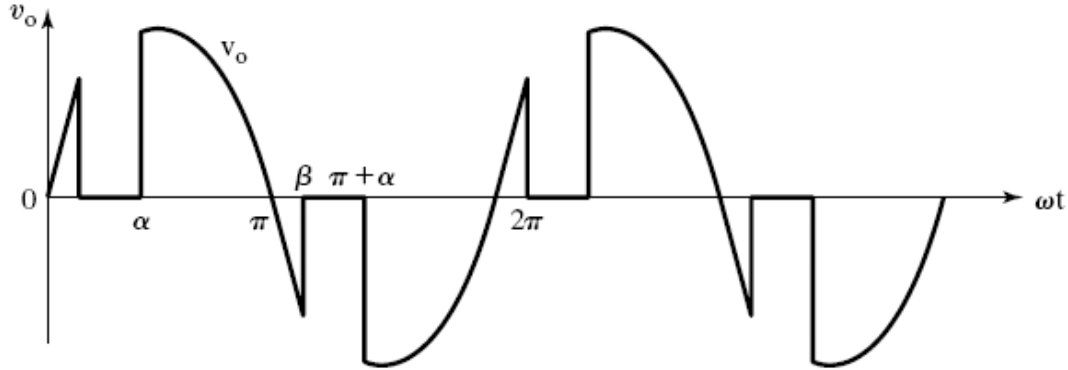**TO DERIVE AN EXPRESSION FOR RMS OUTPUT VOLTAGE  $V_{O(RMS)}$  OF A SINGLE PHASE FULL-WAVE AC VOLTAGE CONTROLLER WITH RL LOAD.**



When  $\alpha > \phi$ , the load current and load voltage waveforms become discontinuous as shown in the figure above.

$$V_{O(RMS)} = \left[ \frac{1}{\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \cdot d(\omega t) \right]^{\frac{1}{2}}$$

Output  $v_o = V_m \sin \omega t$ , for  $\omega t = \alpha$  to  $\beta$ , when  $T_1$  is ON.

$$V_{O(RMS)} = \left[ \frac{V_m^2}{\pi} \int_{\alpha}^{\beta} \frac{(1 - \cos 2\omega t)}{2} d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \left[ \frac{V_m^2}{2\pi} \left\{ \int_{\alpha}^{\beta} d(\omega t) - \int_{\alpha}^{\beta} \cos 2\omega t \cdot d(\omega t) \right\} \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \left[ \frac{V_m^2}{2\pi} \left\{ (\omega t) \Big|_{\alpha}^{\beta} - \left( \frac{\sin 2\omega t}{2} \right) \Big|_{\alpha}^{\beta} \right\} \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \left[ \frac{V_m^2}{2\pi} \left\{ (\beta - \alpha) - \frac{\sin 2\beta}{2} + \frac{\sin 2\alpha}{2} \right\} \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = V_m \left[ \frac{1}{2\pi} \left\{ (\beta - \alpha) + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right\} \right]^{\frac{1}{2}}$$



$$V_{O(RMS)} = \frac{V_m}{\sqrt{2}} \left[ \frac{1}{\pi} \left\{ (\beta - \alpha) + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right\} \right]^{1/2}$$

The RMS output voltage across the load can be varied by changing the trigger angle  $\alpha$ .

For a purely resistive load  $L = 0$ , therefore load power factor angle  $\phi = 0$ .

$$\phi = \tan^{-1} \left( \frac{\omega L}{R} \right) = 0 ;$$

Extinction angle  $\beta = \pi$  radians =  $180^\circ$

### PERFORMANCE PARAMETERS OF A SINGLE PHASE FULL WAVE AC VOLTAGE CONTROLLER WITH RESISTIVE LOAD

- **RMS Output Voltage**  $V_{O(RMS)} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}$  ;  $\frac{V_m}{\sqrt{2}} = V_s =$  RMS input supply voltage.

- $I_{O(RMS)} = \frac{V_{O(RMS)}}{R_L} =$  RMS value of load current.

- $I_s = I_{O(RMS)} =$  RMS value of input supply current.

- **Output load power**


$$P_O = I_{O(RMS)}^2 \times R_L$$

- **Input Power Factor**

$$PF = \frac{P_O}{V_s \times I_s} = \frac{I_{O(RMS)}^2 \times R_L}{V_s \times I_{O(RMS)}} = \frac{I_{O(RMS)} \times R_L}{V_s}$$

$$PF = \frac{V_{O(RMS)}}{V_s} = \sqrt{\frac{1}{\pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}$$

- **Average Thyristor Current,**

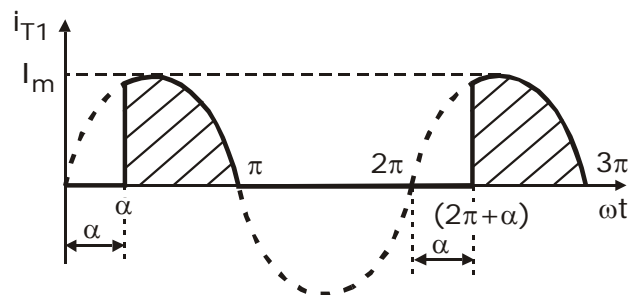

**Fig.: Thyristor Current Waveform**

$$I_{T(Avg)} = \frac{1}{2\pi} \int_{\alpha}^{\pi} i_T d(\omega t) = \frac{1}{2\pi} \int_{\alpha}^{\pi} I_m \sin \omega t d(\omega t)$$

$$I_{T(Avg)} = \frac{I_m}{2\pi} \int_{\alpha}^{\pi} \sin \omega t d(\omega t) = \frac{I_m}{2\pi} \left[ -\cos \omega t \right]_{\alpha}^{\pi}$$

$$I_{T(Avg)} = \frac{I_m}{2\pi} [-\cos \pi + \cos \alpha] = \frac{I_m}{2\pi} [1 + \cos \alpha]$$

- **Maximum Average Thyristor Current, for  $\alpha = 0$ ,**

$$I_{T(Avg)} = \frac{I_m}{\pi}$$

- **RMS Thyristor Current**

$$I_{T(RMS)} = \sqrt{\frac{1}{2\pi} \left[ \int_{\alpha}^{\pi} I_m^2 \sin^2 \omega t d(\omega t) \right]}$$

$$I_{T(RMS)} = \frac{I_m}{\sqrt{2}} \sqrt{\frac{1}{2\pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}$$

- **Maximum RMS Thyristor Current, for  $\alpha = 0$ ,**

$$I_{T(RMS)} = \frac{I_m}{2}$$

In the case of a single phase full wave ac voltage controller circuit using a Triac with resistive load, the average thyristor current  $I_{T(Avg)} = 0$ . Because the Triac conducts in both the half cycles and the thyristor current is alternating and we obtain a symmetrical thyristor current waveform which gives an average value of zero on integration.

## PERFORMANCE PARAMETERS OF A SINGLE PHASE FULL WAVE AC VOLTAGE CONTROLLER WITH R-L LOAD

### The Expression for the Output (Load) Current

The expression for the output (load) current which flows through the thyristor, during  $\omega t = \alpha$  to  $\beta$  is given by

$$i_o = i_{T_1} = \frac{V_m}{Z} \left[ \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right] ; \quad \text{for } \alpha \leq \omega t \leq \beta$$

Where,

$V_m = \sqrt{2}V_s$  = Maximum or peak value of input ac supply voltage.

$Z = \sqrt{R^2 + (\omega L)^2}$  = Load impedance.

$$\phi = \tan^{-1}\left(\frac{\omega L}{R}\right) = \text{Load impedance angle (load power factor angle)}.$$

$\alpha$  = Thyristor trigger angle = Delay angle.

$\beta$  = Extinction angle of thyristor, (value of  $\omega t$ ) at which the thyristor (load) current falls to zero.

$\beta$  is calculated by solving the equation

$$\sin(\beta - \phi) = \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\beta - \alpha)}$$

**Thyristor Conduction Angle**  $\delta = (\beta - \alpha)$

Maximum thyristor conduction angle  $\delta = (\beta - \alpha) = \pi$  radians =  $180^\circ$  for  $\alpha \leq \phi$ .

**RMS Output Voltage**

$$V_{O(RMS)} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} \left[ (\beta - \alpha) + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right]}$$

**The Average Thyristor Current**

$$I_{T(Avg)} = \frac{1}{2\pi} \left[ \int_{\alpha}^{\beta} i_{T_1} d(\omega t) \right]$$

$$I_{T(Avg)} = \frac{1}{2\pi} \left[ \int_{\alpha}^{\beta} \frac{V_m}{Z} \left[ \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right] d(\omega t) \right]$$

$$I_{T(Avg)} = \frac{V_m}{2\pi Z} \left[ \int_{\alpha}^{\beta} \sin(\omega t - \phi) . d(\omega t) - \int_{\alpha}^{\beta} \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} d(\omega t) \right]$$

Maximum value of  $I_{T(Avg)}$  occur at  $\alpha = 0$ . The thyristors should be rated for maximum  $I_{T(Avg)} = \left(\frac{I_m}{\pi}\right)$ , where  $I_m = \frac{V_m}{Z}$ .

**RMS Thyristor Current**  $I_{T(RMS)}$

$$I_{T(RMS)} = \sqrt{\left[ \frac{1}{2\pi} \int_{\alpha}^{\beta} i_{T_1}^2 d(\omega t) \right]}$$

Maximum value of  $I_{T(RMS)}$  occurs at  $\alpha = 0$ . Thyristors should be rated for maximum  $I_{T(RMS)} = \left(\frac{I_m}{2}\right)$

When a Triac is used in a single phase full wave ac voltage controller with RL type of load, then  $I_{T(Avg)} = 0$  and maximum  $I_{T(RMS)} = \frac{I_m}{\sqrt{2}}$

### PROBLEMS

1. A single phase full wave ac voltage controller supplies an RL load. The input supply voltage is 230V, RMS at 50Hz. The load has  $L = 10\text{mH}$ ,  $R = 10\Omega$ , the delay angle of thyristors  $T_1$  and  $T_2$  are equal, where  $\alpha_1 = \alpha_2 = \frac{\pi}{3}$ . Determine
  - a. Conduction angle of the thyristor  $T_1$ .
  - b. RMS output voltage.
  - c. The input power factor.
 Comment on the type of operation.
2. A single phase full wave controller has an input voltage of 120 V (RMS) and a load resistance of 6 ohm. The firing angle of thyristor is  $\pi/2$ . Find
  - a. RMS output voltage
  - b. Power output
  - c. Input power factor
  - d. Average and RMS thyristor current.
3. A single phase half wave ac regulator using one SCR in anti-parallel with a diode feeds 1 kW, 230 V heater. Find load power for a firing angle of  $45^\circ$ .
4. Find the RMS and average current flowing through the heater shown in figure. The delay angle of both the SCRs is  $45^\circ$ .

